

## Lab-7 CSE 209

Pre Lab Report


DC Circuit

$$R_L = R_{Th} \text{ (Maximum Power)}$$

then product of  
 $I_L$  and  $V_L$  will be  
maximum


$$\boxed{P_{max} = I_L \times V_L}$$
$$= \frac{V_{th}^2}{4R_{Th}}$$

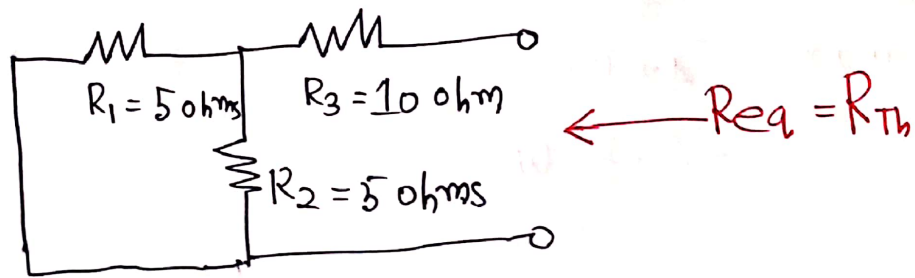when we calculate  $R_{Th}$  then we disconnect the load and turn off all the independent sources.



$$\begin{aligned}
 R_{Th} &= [5 \parallel 5] + 10 \Omega \\
 &= (2.5 + 10) \Omega \\
 &= 12.5 \Omega
 \end{aligned}$$

Here  $R_3$  Resistor is floating

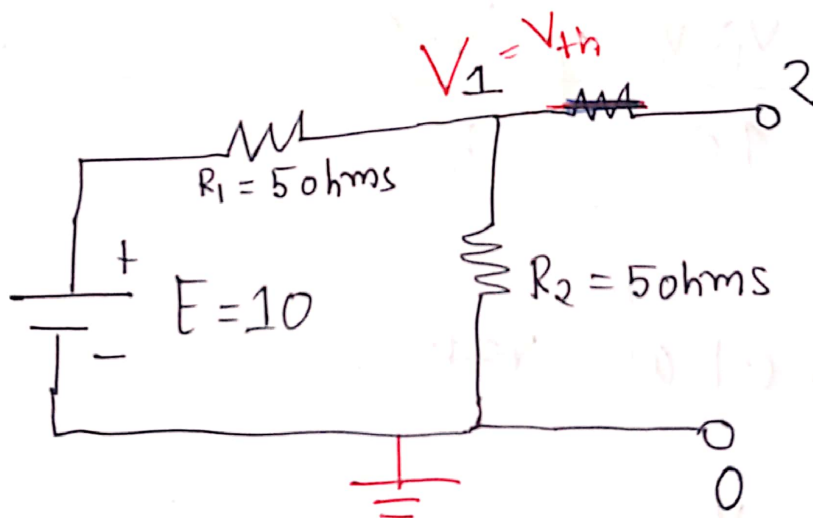


$$V_{Th} = V_{2,0} = V_1 = 5 \text{ V}$$

using VDR

$$V_1 = \frac{5 \times 10}{5 + 5} = \frac{50}{10} = 5 \text{ V}$$
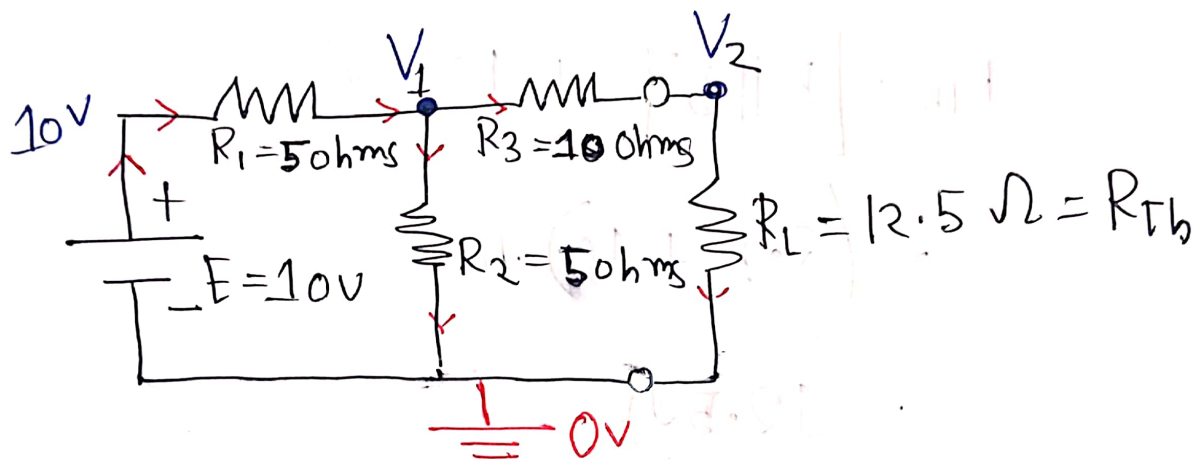
$$P_{\max} = \frac{5^2}{4 \times 12.5} = 0.5 \text{ W}$$



Applying KCL at node 1

$$\frac{10 - V_1}{5} = \frac{V_1 - V_2}{10} + \frac{V_1 - 0}{5} \quad (1)$$

Applying KCL at node 2

$$\frac{V_1 - V_2}{10} = \frac{V_2 - 0}{12.5} \quad (11)$$

Solving equation (1) and (2) we get

$$V_1 = \frac{9}{2} V = 4.5 V$$

$$V_2 = \frac{5}{2} V = 2.5 V$$

$$\begin{aligned} I(R_3) &= \frac{V_1 - V_2}{10} \\ &= \frac{4.5 - 2.5}{10} \\ &= \frac{2}{10} \\ &= \frac{1}{5} \text{ A} \end{aligned}$$

or,

$$\begin{aligned} I(R_3) &= \frac{V_2}{12.5} \\ &= \frac{2.5}{12.5} \\ &= \frac{1}{5} \text{ A} \end{aligned}$$