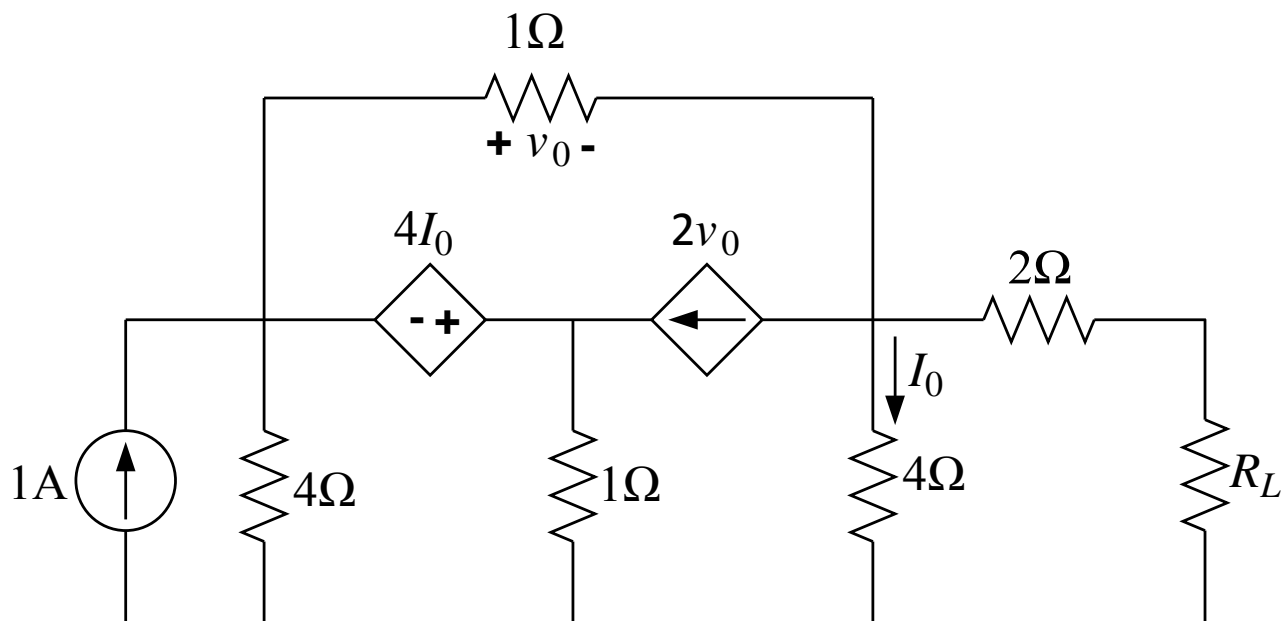


# CSE 209 Electrical Circuits

## Project

### PSpice Analysis for Maximum Power Transfer

1. Using PSpice Simulation, determine the Thevenin's equivalent of the circuit looking from the load resistance  $R_L$ .
2. From the Thevenin's equivalent circuit, theoretically determine the value of load resistance  $R_L$  for maximum power transfer. Using PSpice Simulation of the Thevenin's equivalent circuit with  $R_L$  for maximum power transfer, determine the value of maximum power transferred to  $R_L$ .
3. Using PSpice Simulation with resistance sweep, determine the value of  $R_L$  for maximum power transfer and the corresponding maximum power.
4. Compare the value of  $R_L$  and maximum power obtained in steps 2 and 3.



### Marks Distribution

Assessment Area	Mark
<b>C3: Cognitive: Applying</b>	12
<b>P2: Psychomotor: Manipulation</b>	1
<b>P3: Psychomotor: Precision</b>	1
<b>A2: Affective: Responding</b>	1
<b>Total</b>	<b>15</b>